

Determine the feedback ratio $\beta = \frac{V_n}{V_o}$

① The right amplifier, A2 : constant mode


$$i_{ref} = \text{constant} = \frac{V_{ref}}{R_{ref}}$$

$$V_r = \text{constant}$$

② small signal analysis

- voltage source \Rightarrow ground \oplus

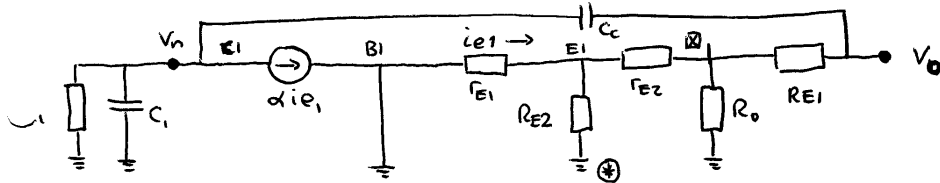- current source \Rightarrow open circuit \boxtimes




determine i_{e1} :

$$i_{e1} = -V_n \cdot R_{eq}$$

$$i_{ref} = \frac{V_{ref}}{R_{ref}} = \frac{10V}{1k\Omega} = 10\mu A, \quad r_{E2} = \frac{V_T}{i_{ref}} = \frac{26mV}{10\mu A} = 2.6\Omega$$

$$\max i_1 = \frac{V_{max}}{R_1} = \frac{10V}{1k\Omega} = 10\mu A, \quad r_{E1} = 2.6\Omega$$

②/4

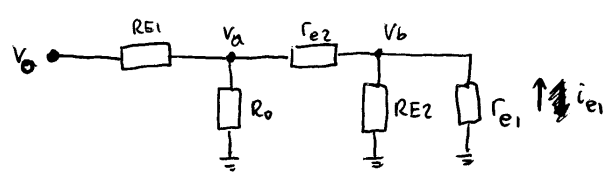

$R_{E1} = 10\text{ k}$
 $R_{E2} = 10\text{ k}$
 $R_o = 10\text{ k}$
 $r_{e1} = r_{e2} = 2.6\ \Omega$

$$V_a = V_0 \cdot \frac{R_x}{R_x + R_{E1}} \quad R_x = R_o \parallel (r_{e2} + R_{E2} \parallel r_{e1})$$

$$R_x = 10\text{ k} \parallel (2.6\ \Omega + 10\text{ k} \parallel 2.6\ \Omega)$$

$$= 10\text{ k} \parallel 5.2\ \Omega$$

$$= 5.2\ \Omega$$

$$V_a = V_0 \cdot \frac{5.2}{5.2 + 10\text{ k}} = 5.2 \cdot 10^{-4} V_n$$


$$V_b = V_a \cdot \frac{R_y}{R_y + r_{e2}} \quad R_y = R_{E2} \parallel r_{e1} \quad r_{e1} = 2.6\ \Omega$$

$$V_b = V_a \cdot \frac{2.6}{2.6 + 2.6} = 0.5 V_a = 0.5 \times 5.2 \cdot 10^{-4} V_0$$

$$= 2.6 \cdot 10^{-4} V_0$$

$V_b \approx \frac{r_{e1}}{R_{E1}} \cdot V_n$
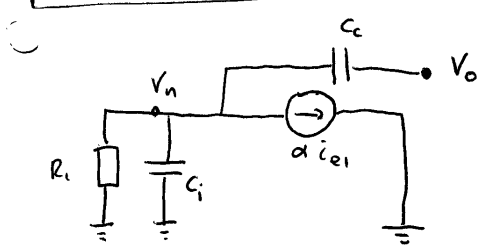
$$i_{e1} = -\frac{V_b}{r_{e1}} = -\frac{V_0}{R_{E1}}$$



$I_n \quad V_n : \sum I = 0$

$$V_n \left(\frac{1}{R_1} + sC_1 \right) + (V_n - V_0) sC_c - V_0 \frac{1}{R_{E1}} = 0$$

$$\beta = \frac{V_n}{V_0} = \frac{\frac{1}{R_{E1}} + sC_c}{\frac{1}{R_1} + sC_1 + sC_c} = \frac{R_1}{R_{E1}} \cdot \frac{1 + sR_{E1}C_c}{1 + sR_1(C_1 + C_c)}$$

$R_1 = 1\text{ k}\Omega$
 $C_1 = 10\text{ pF}$
 $C_c = 1\text{ nF}$
 $R_{E1} = 10\text{ k}\Omega$

$\beta_0 = 0.1$

pole at


$$f_p = \frac{1}{2\pi R_1 (C_1 + C_c)}$$

158 kHz

zero at

$$f_0 = \frac{1}{2\pi R_{E1} C_c}$$

15.9 kHz

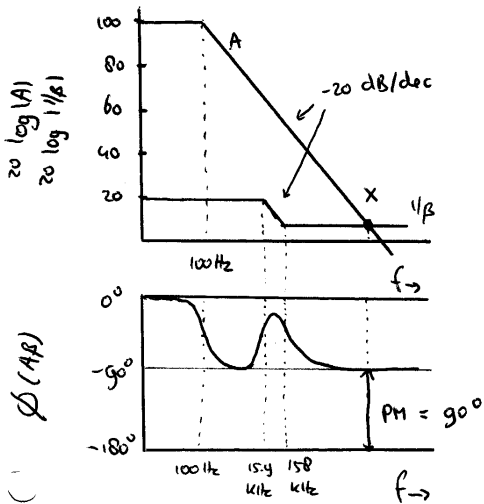

$$\beta = \frac{R_1}{R_{E1}} \cdot \frac{1 + s R_{E1} C_c}{1 + s R_1 (C_1 + C_c)}$$

$$\beta(f=0) = \frac{R_1}{R_{E1}} = 0.1$$

$$\beta(f=\infty) = \frac{R_1}{R_{E1}} \cdot \frac{R_{E1} C_c}{R_1 (C_1 + C_c)} \approx 1$$

f_x :

$$|A| = \frac{A_0}{(1 + f_x/f_p)} \approx A_0 \frac{f_p}{f_x}$$

at X: $|A| = |\beta(f=\infty)|$

$$A_0 \frac{f_p}{f_x} = \beta_\infty = 1 \Rightarrow f_x = A_0 f_p$$

$$= 10^7 \text{ Hz} = 10 \text{ MHz}$$


In reality, this circuit is probably not stable due to the fact that the OpAmp will have more poles before 10 MHz.

stability of right part of circuit

left amplifier A1 constant mode


$$i_i = \text{constant} (= v_{max}/R_1)$$

$$V_{o1} = \text{constant}$$

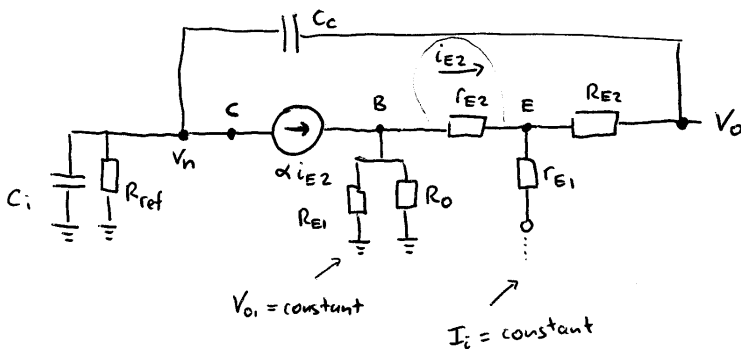

$$\alpha = 1$$

Kirchhoff in B ($\alpha=1$)

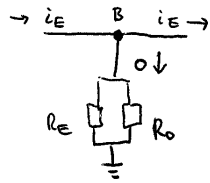

No current through $R_E // R_O \Rightarrow V_B = 0V$

$$i_{E2} = \frac{V_B - V_O}{R_{E2} + r_{E2}} = -\frac{V_O}{R_{E2} + r_{E2}} = -\frac{V_O}{R'_{E2}}$$

$\sum I_n V_n : \sum I = 0$

$$V_n \left(\frac{1}{R_{ref}} + sC_i \right) + \alpha i_{E2} + sC_c (V_n - V_o) = 0$$

$$V_n \left(\frac{1}{R_{ref}} + sC_i \right) - V_o \left(\frac{1}{R'_E} \right) + sC_c (V_n - V_o) = 0$$

$$\beta = \frac{V_n}{V_o} = \frac{\frac{1}{R'_E} + sC_c}{\frac{1}{R_{ref}} + sC_i + sC_c} = \frac{R_{ref} \cdot (1 + sR'_E C_c)}{R'_E (1 + sR_{ref} (C_i + C_c))}$$

$\beta_0 = 0.1$

poles at $f_p = \frac{1}{2\pi R_{ref} (C_i + C_c)}$
158 kHz

zero at $f_o = \frac{1}{2\pi R'_E C_c}$
15.9 kHz

equal to (a)

